Fuel Pump Circuit Troubleshooting Flow Charts

Author: Paul B. Anders email: paul.b.anders@intel.com Version: 1.0

There are five flowcharts in this troubleshooting checklist that cover all of the circuits that control the operation of the fuel pump. A diagram of the relay board is included to assist in identifying the relays, board traces, connectors and wiring. Start at the "Problem Isolation" chart and work your way through. The navigation tool at the bottom will let you move from chart to chart. Clicking on the red or green termination ovals will either take you to the next flowchart or to the fault descriptions.













